

*Ain Shams University  
Faculty of Engineering  
Electronics and Communication Department  
ECE 342: Digital Circuits  
3rd Year Communications*



## ***Arithmetic and Logical Unit Design Project***


| <b><i>NAME</i></b>               | <b><i>CODE</i></b> |
|----------------------------------|--------------------|
| <i>Moataz Mokhtar Said</i>       | <i>1701460</i>     |
| <i>Farid Mohammed Farid</i>      | <i>1700985</i>     |
| <i>Ahmed Ayman Ahmed</i>         | <i>1700037</i>     |
| <i>Mohamed Ashraf Farouk</i>     | <i>1701154</i>     |
| <i>Yumna Ahmed Mohammed</i>      | <i>1701692</i>     |
| <i>Youssef Ayman El-Rouby</i>    | <i>1701709</i>     |
| <i>Nour Mahmoud Galal</i>        | <i>1701587</i>     |
| <i>Abdelrahman Mohamed Anwar</i> | <i>1700757</i>     |
| <i>Mahmoud Mohamed Hanafy</i>    | <i>1701360</i>     |
| <i>Salma Tarek El-Alfy</i>       | <i>1700620</i>     |

## Contents

|   |    |
|---|----|
| <b>Circuit Schematics:</b> .....                                | 3  |
| <b>CMOS Inverter:</b> .....                                     | 3  |
| <b>NAND Gate:</b> .....   | 3  |
| <b>NOR Gate:</b> .....  | 4  |
| <b>AND Gate:</b> .....  | 4  |
| <b>OR Gate:</b> .....   | 5  |
| <b>XOR Gate:</b> .....  | 5  |
| <b>XNOR Gate:</b> .....   | 6  |
| <b>2-1 Multiplexer:</b> .....                                   | 6  |
| <b>8-1 Multiplexer:</b> .....                                   | 7  |
| <b>1-bit Logical Operator MUX:</b> .....                        | 7  |
| <b>4-bit Logical Operator MUX:</b> .....                        | 8  |
| <b>1-bit Adder:</b> .....                                       | 8  |
| <b>4-bit Adder:</b> .....                                       | 9  |
| <b>4-bit Multiplier:</b> .....                                  | 9  |
| <b>Arithmetic unit operations without multiplication:</b> ..... | 10 |
| <b>Arithmetic unit:</b> .....                                   | 10 |
| <b>Arithmetic and logical unit:</b> .....                       | 11 |
| <b>ALU Operations:</b> .....                                    | 12 |
| <b>Delay and Power Consumption:</b> .....                       | 17 |
| <b>Delay:</b> .....   | 17 |
| <b>At Rising Edges:</b> .....                                   | 17 |
| <b>At Rising Edges:</b> .....                                   | 17 |
| <b>Power Consumption:</b> .....                                 | 18 |
| <b>VHDL Code:</b> .....   | 19 |
| <b>VHDL Test Benching:</b> .....                                | 21 |


# Circuit Schematics:

CMOS Inverter:

 


Reference sizing relative to CMOS inverter 2:1.


NAND Gate:

 


### NOR Gate:

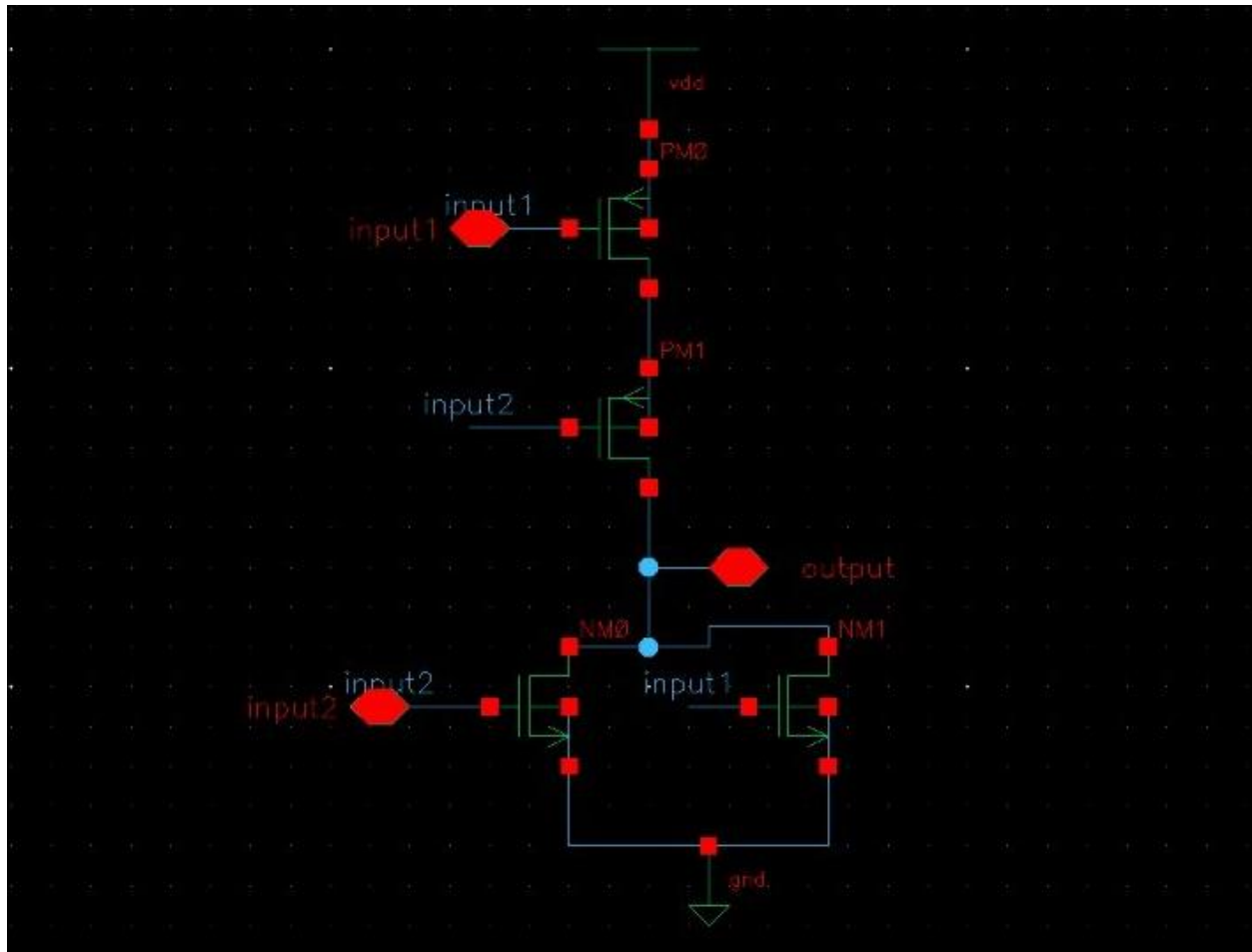


### AND Gate:

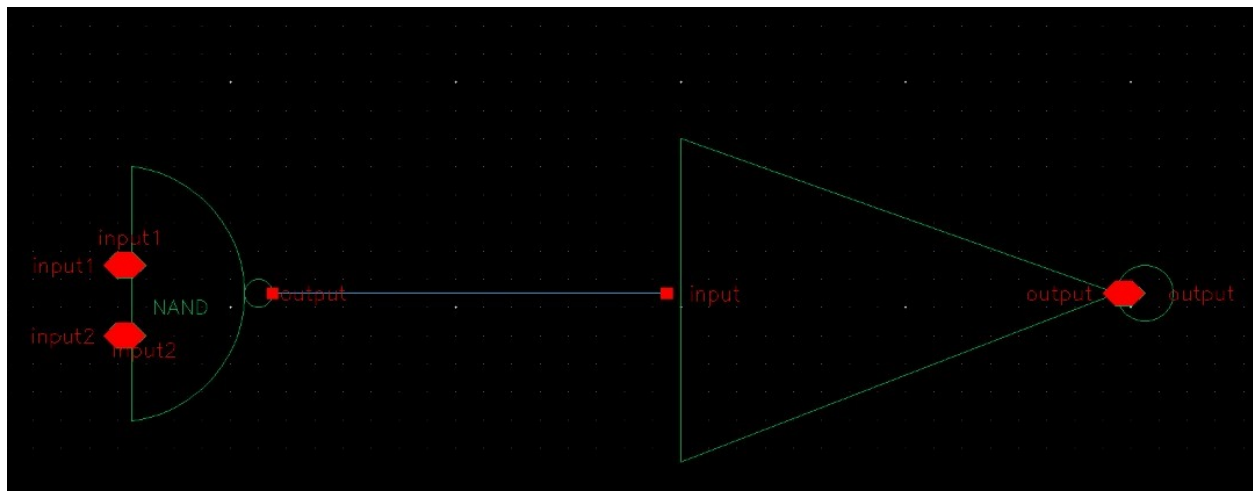


### OR Gate:

 


### XOR Gate:

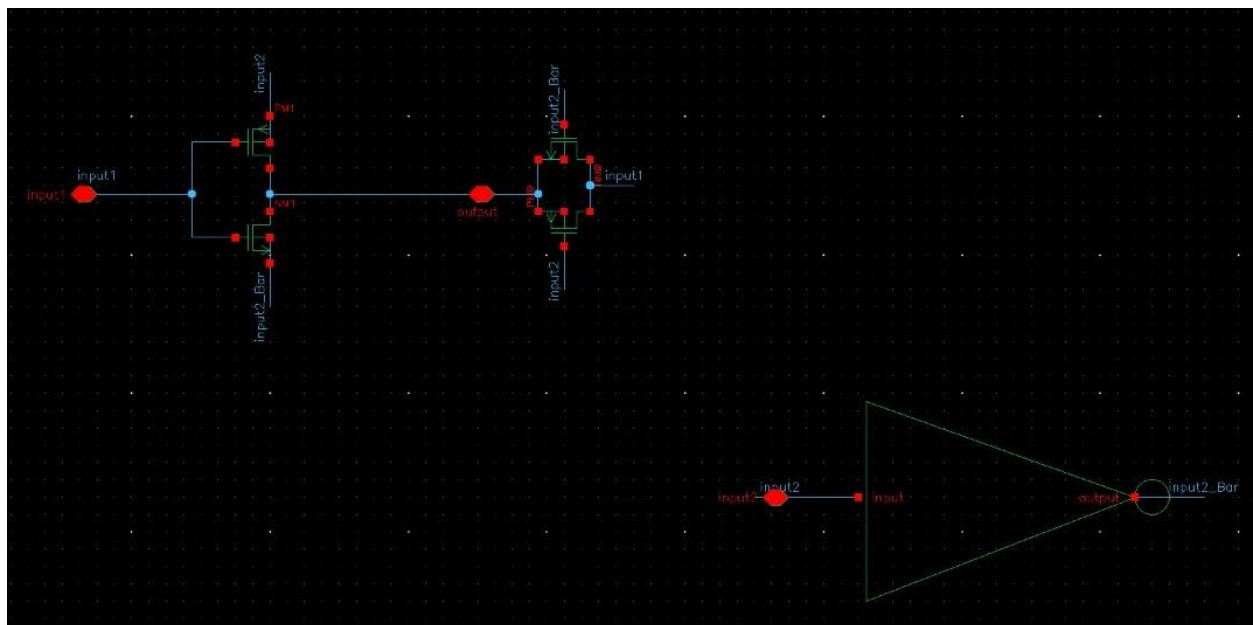


### *XNOR Gate:*

 


### *2-1 Multiplexer:*

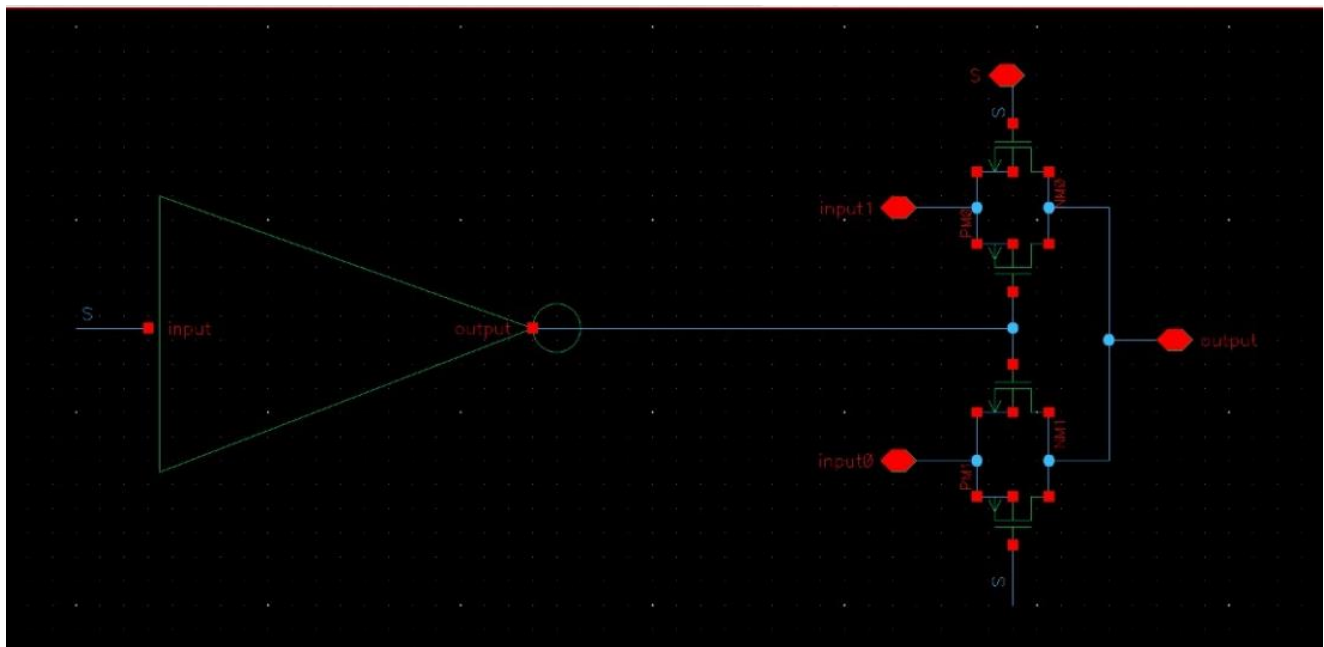

## 8-1 Multiplexer:

 


## 1-bit Logical Operator MUX:

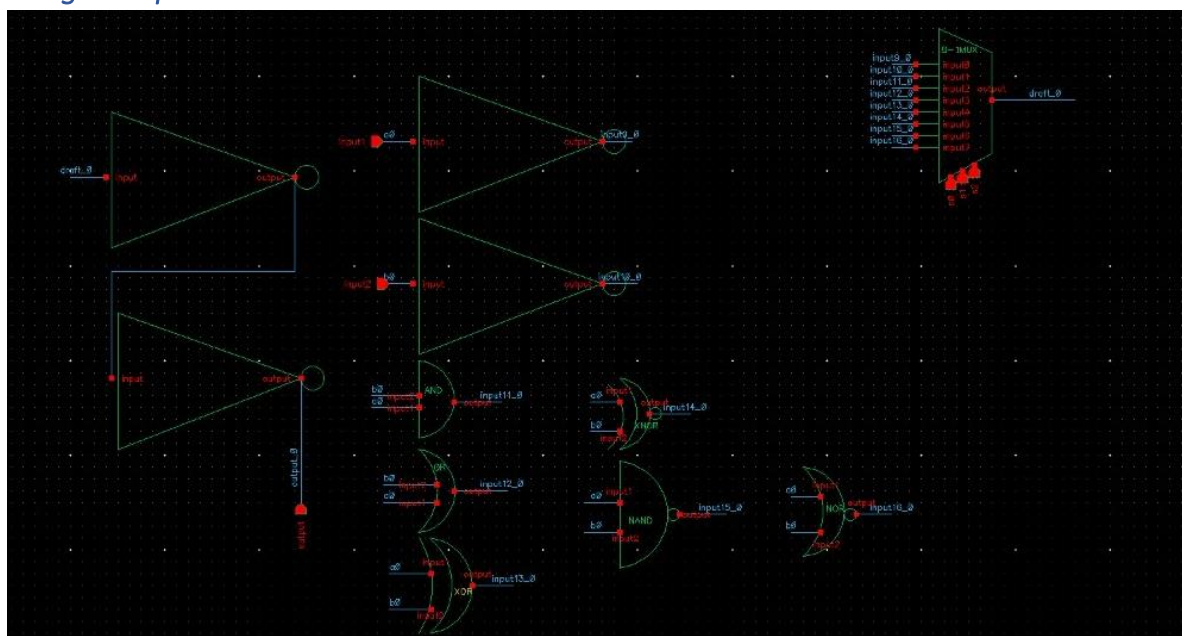


Note: We put 2 CMOS inverter after the output of the mux because our output wasn't rail to rail.

#### 4-bit Logical Operator MUX:

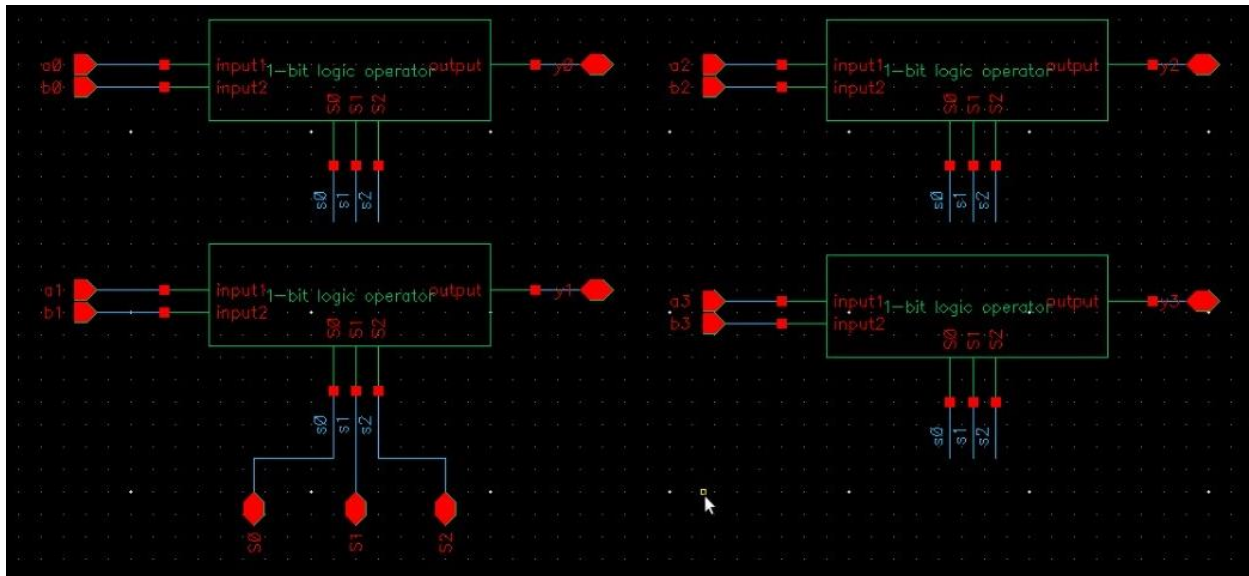


#### 1-bit Adder:

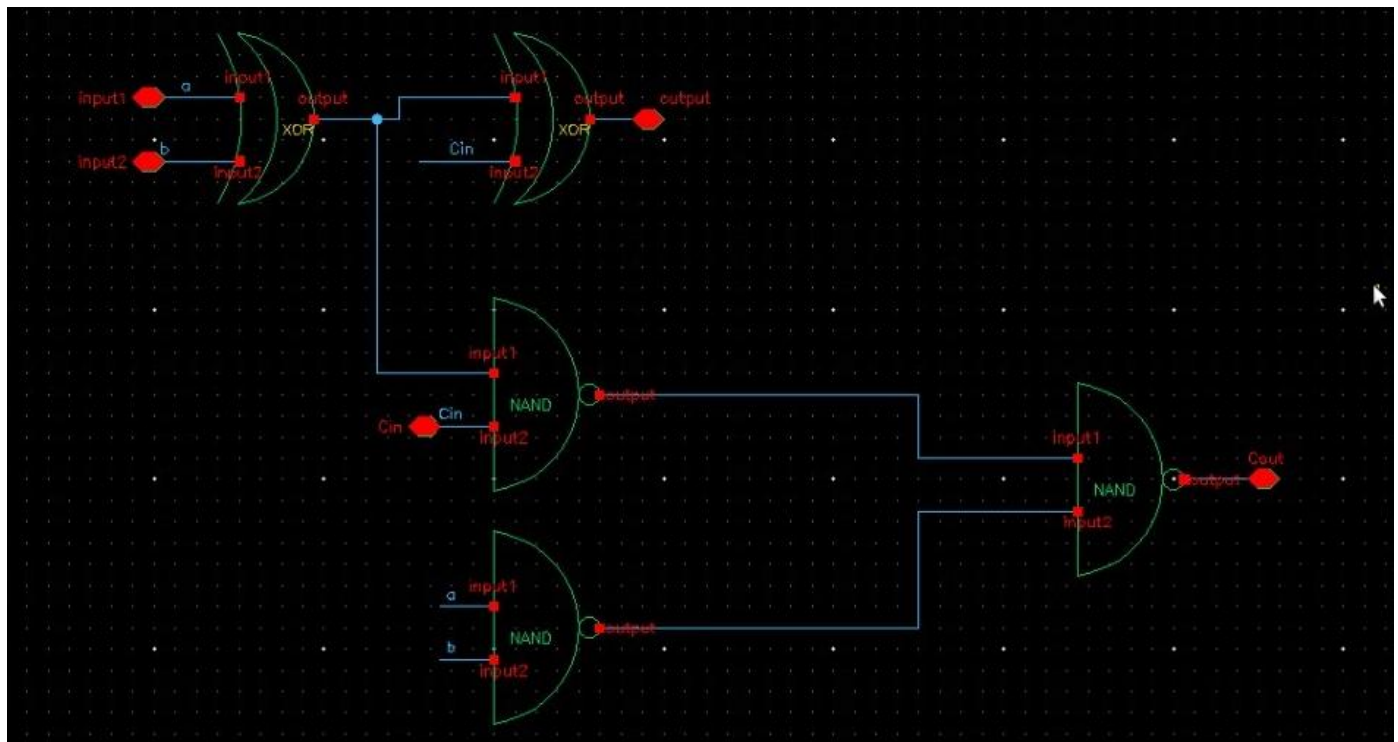





4-bit Adder:

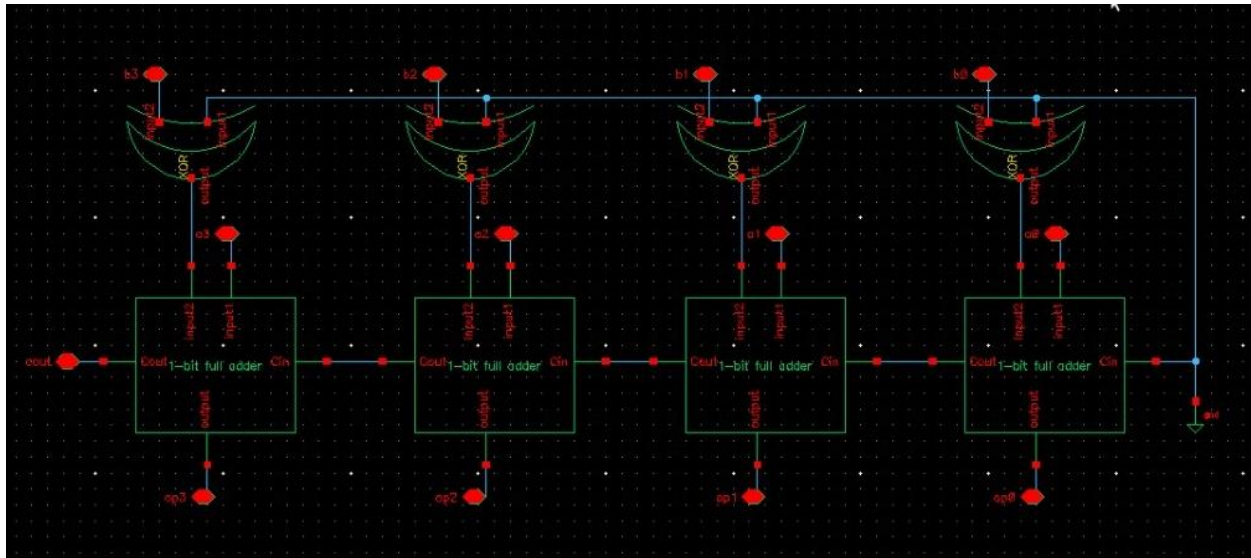


4-bit Multiplier:

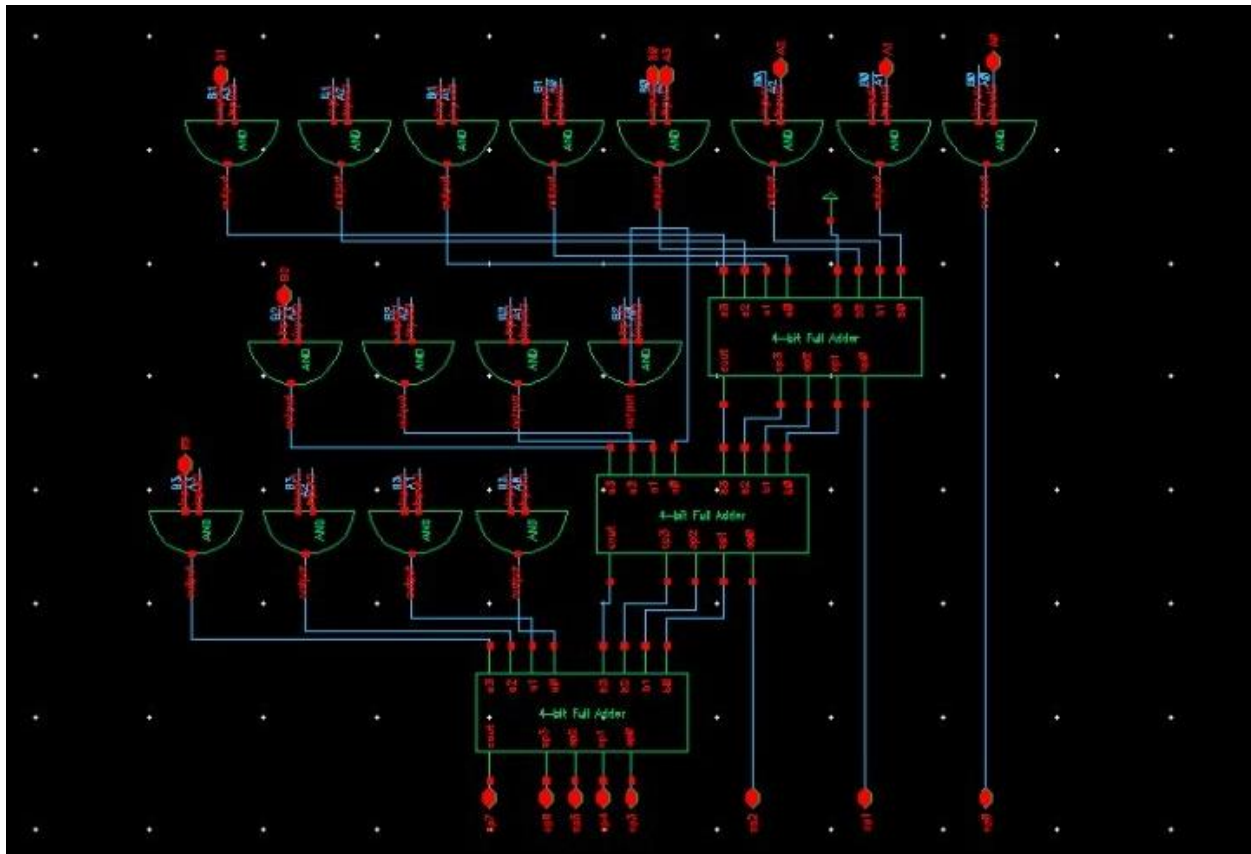

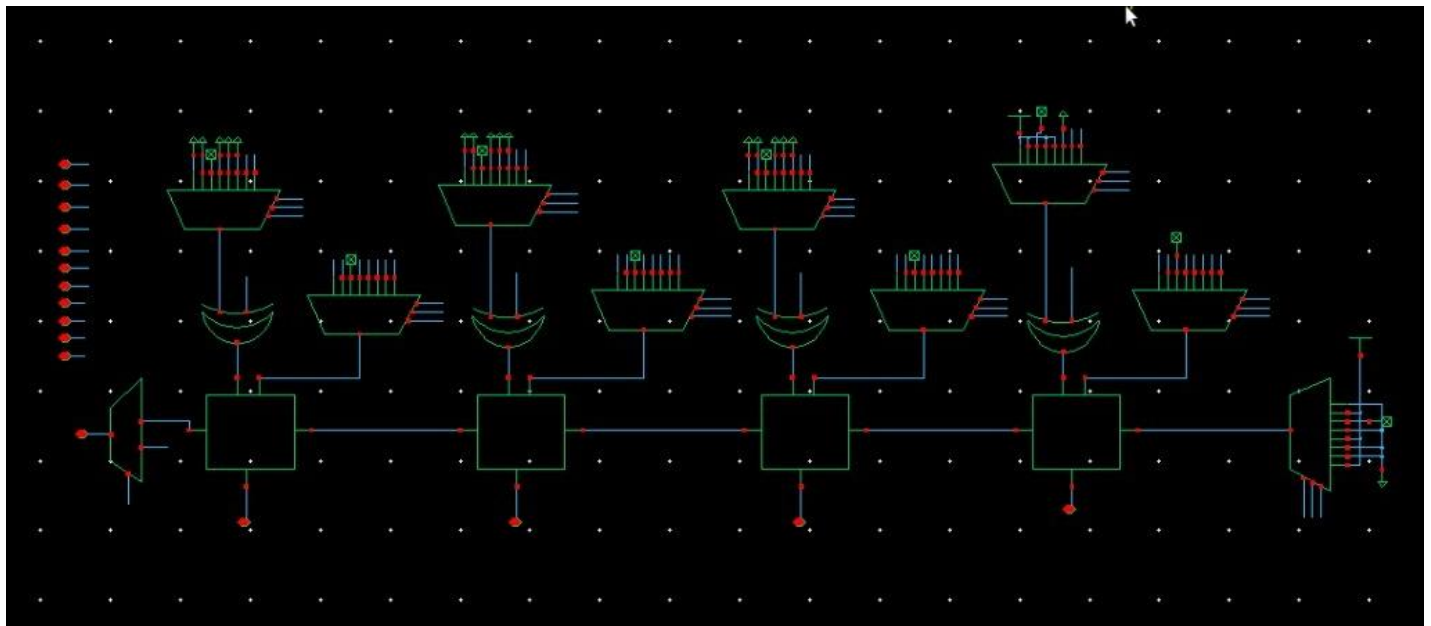
### Arithmetic unit operations without multiplication:



### Arithmetic unit:

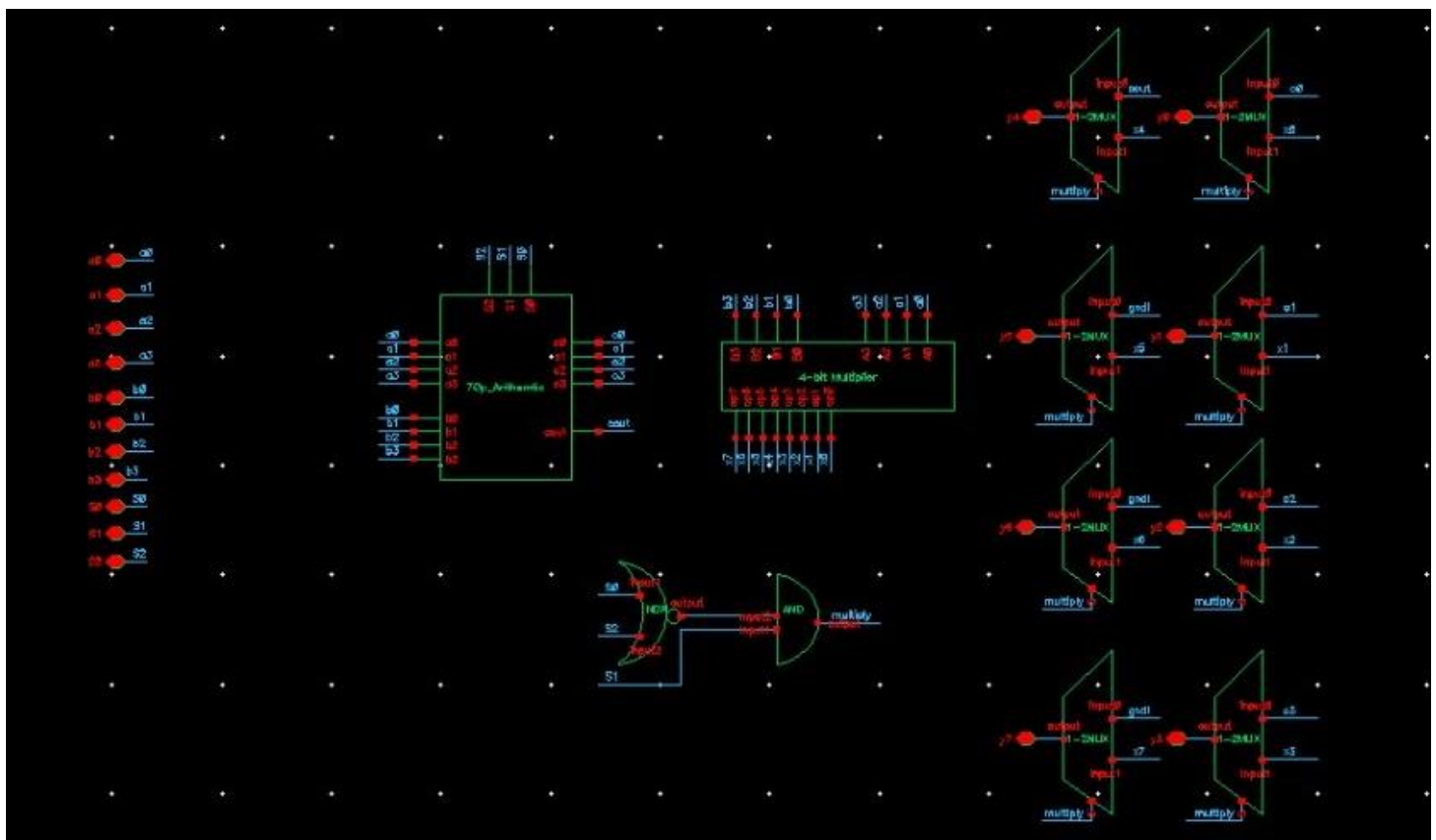

## Arithmetic and logical unit:

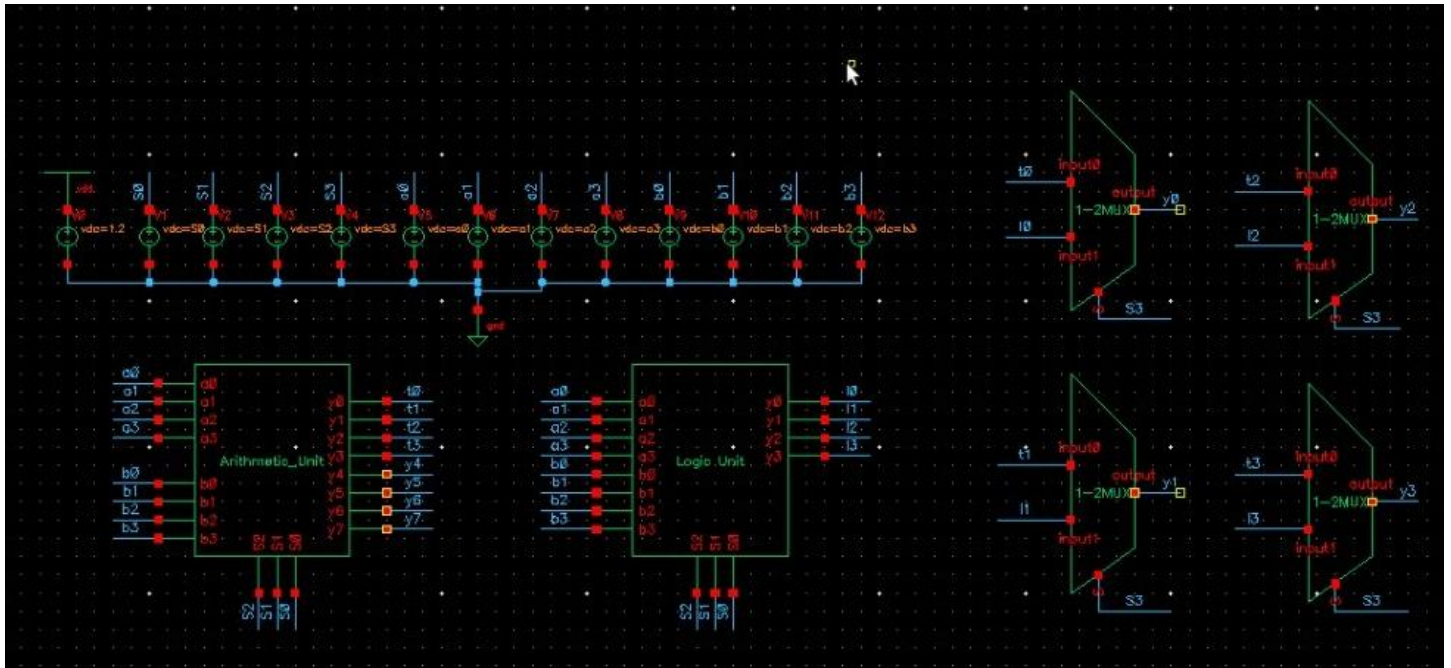

# ALU Operations:

Arithmetic Operation

Input A = 9 (00001001)

Input B=5 (00000101)

Output Y (8 bits) =( Y7 Y6 Y5 Y4 Y3 Y2 Y1 Y0 )

DC-Analysis

|                      |                 |            |         |                 |
|----------------------|-----------------|------------|---------|-----------------|
| 0000<br><i>inc a</i> | Test            | Output     | Nominal | 0               |
|                      | Digital:Test1:1 | VDC("/y0") | 23.52u  | 1               |
|                      | Digital:Test1:1 | VDC("/y1") | 1.2     | 0               |
|                      | Digital:Test1:1 | VDC("/y2") | 29.12u  | 1               |
|                      | Digital:Test1:1 | VDC("/y3") | 1.2     | 0               |
|                      | Digital:Test1:1 | VDC("/y4") | 2.906u  | 0               |
|                      | Digital:Test1:1 | VDC("/y5") | 2.309u  | 0               |
|                      | Digital:Test1:1 | VDC("/y6") | 25.56p  | 0               |
|                      | Digital:Test1:1 | VDC("/y7") | 13.16p  | 0               |
|                      |                 |            |         | Decimal<br>= 10 |
| 0001<br><i>dec a</i> | Test            | Output     | Nominal | 0               |
|                      | Digital:Test1:1 | VDC("/y0") | 18.66u  | 0               |
|                      | Digital:Test1:1 | VDC("/y1") | 11.8u   | 0               |
|                      | Digital:Test1:1 | VDC("/y2") | 18.74u  | 1               |
|                      | Digital:Test1:1 | VDC("/y3") | 1.2     | 0               |
|                      | Digital:Test1:1 | VDC("/y4") | 2.351u  | 0               |
|                      | Digital:Test1:1 | VDC("/y5") | 2.309u  | 0               |
|                      | Digital:Test1:1 | VDC("/y6") | 25.56p  | 0               |
|                      | Digital:Test1:1 | VDC("/y7") | 13.16p  | 0               |
|                      |                 |            |         | Decimal<br>= 8  |
| 0010<br><i>a * b</i> | Test            | Output     | Nominal | 1               |
|                      | Digital:Test1:1 | VDC("/y0") | 1.2     | 0               |
|                      | Digital:Test1:1 | VDC("/y1") | 6.618u  | 1               |
|                      | Digital:Test1:1 | VDC("/y2") | 1.2     | 1               |
|                      | Digital:Test1:1 | VDC("/y3") | 1.2     | 0               |
|                      | Digital:Test1:1 | VDC("/y4") | 6.236u  | 1               |
|                      | Digital:Test1:1 | VDC("/y5") | 1.2     | 0               |
|                      | Digital:Test1:1 | VDC("/y6") | 5.646u  | 0               |
|                      | Digital:Test1:1 | VDC("/y7") | 2.905u  | 0               |
|                      |                 |            |         | Decimal<br>= 45 |

0011  
*inc b*

| Test            | Output     | Nominal |
|-----------------|------------|---------|
| Digital:Test1:1 | VDC("/y0") | 23.52u  |
| Digital:Test1:1 | VDC("/y1") | 1.2     |
| Digital:Test1:1 | VDC("/y2") | 1.199   |
| Digital:Test1:1 | VDC("/y3") | 650u    |
| Digital:Test1:1 | VDC("/y4") | 2.905u  |
| Digital:Test1:1 | VDC("/y5") | 2.309u  |
| Digital:Test1:1 | VDC("/y6") | 25.56p  |
| Digital:Test1:1 | VDC("/y7") | 13.16p  |

|                |
|----------------|
| 0              |
| 1              |
| 1              |
| 0              |
| 0              |
| 0              |
| 0              |
| 0              |
| Decimal<br>= 6 |

0100  
*dec b*

| Test            | Output     | Nominal |
|-----------------|------------|---------|
| Digital:Test1:1 | VDC("/y0") | 18.61u  |
| Digital:Test1:1 | VDC("/y1") | 11.87u  |
| Digital:Test1:1 | VDC("/y2") | 1.2     |
| Digital:Test1:1 | VDC("/y3") | 18.76u  |
| Digital:Test1:1 | VDC("/y4") | 2.4u    |
| Digital:Test1:1 | VDC("/y5") | 2.309u  |
| Digital:Test1:1 | VDC("/y6") | 25.56p  |
| Digital:Test1:1 | VDC("/y7") | 13.16p  |

|                |
|----------------|
| 0              |
| 0              |
| 1              |
| 0              |
| 0              |
| 0              |
| 0              |
| 0              |
| Decimal<br>= 4 |

0101  
*transfer  
a*

| Test            | Output     | Nominal |
|-----------------|------------|---------|
| Digital:Test1:1 | VDC("/y0") | 1.2     |
| Digital:Test1:1 | VDC("/y1") | 8.04u   |
| Digital:Test1:1 | VDC("/y2") | 338.1u  |
| Digital:Test1:1 | VDC("/y3") | 1.199   |
| Digital:Test1:1 | VDC("/y4") | 2.906u  |
| Digital:Test1:1 | VDC("/y5") | 2.309u  |
| Digital:Test1:1 | VDC("/y6") | 25.56p  |
| Digital:Test1:1 | VDC("/y7") | 13.16p  |

|                |
|----------------|
| 1              |
| 0              |
| 0              |
| 1              |
| 0              |
| 0              |
| 0              |
| 0              |
| Decimal<br>= 9 |



0110  
add a,b

| Test            | Output     | Nominal |
|-----------------|------------|---------|
| Digital:Test1:1 | VDC("/y0") | 23.52u  |
| Digital:Test1:1 | VDC("/y1") | 1.2     |
| Digital:Test1:1 | VDC("/y2") | 1.199   |
| Digital:Test1:1 | VDC("/y3") | 1.199   |
| Digital:Test1:1 | VDC("/y4") | 2.906u  |
| Digital:Test1:1 | VDC("/y5") | 2.309u  |
| Digital:Test1:1 | VDC("/y6") | 25.56p  |
| Digital:Test1:1 | VDC("/y7") | 13.16p  |

|                 |
|-----------------|
| 0               |
| 1               |
| 1               |
| 1               |
| 0               |
| 0               |
| 0               |
| 0               |
| Decimal<br>= 14 |


0111  
sub a,b

| Test            | Output     | Nominal |
|-----------------|------------|---------|
| Digital:Test1:1 | VDC("/y0") | 18.55u  |
| Digital:Test1:1 | VDC("/y1") | 11.98u  |
| Digital:Test1:1 | VDC("/y2") | 1.2     |
| Digital:Test1:1 | VDC("/y3") | 23.34u  |
| Digital:Test1:1 | VDC("/y4") | 2.471u  |
| Digital:Test1:1 | VDC("/y5") | 2.309u  |
| Digital:Test1:1 | VDC("/y6") | 25.56p  |
| Digital:Test1:1 | VDC("/y7") | 13.16p  |


|                |
|----------------|
| 0              |
| 0              |
| 1              |
| 0              |
| 0              |
| 0              |
| 0              |
| 0              |
| Decimal<br>= 4 |

Logic Operations  
Waveform testing  
Transient Analysis

1000  
 $\bar{a}$

 


1001  
 $\bar{b}$

 

1010  
AND




1011  
OR

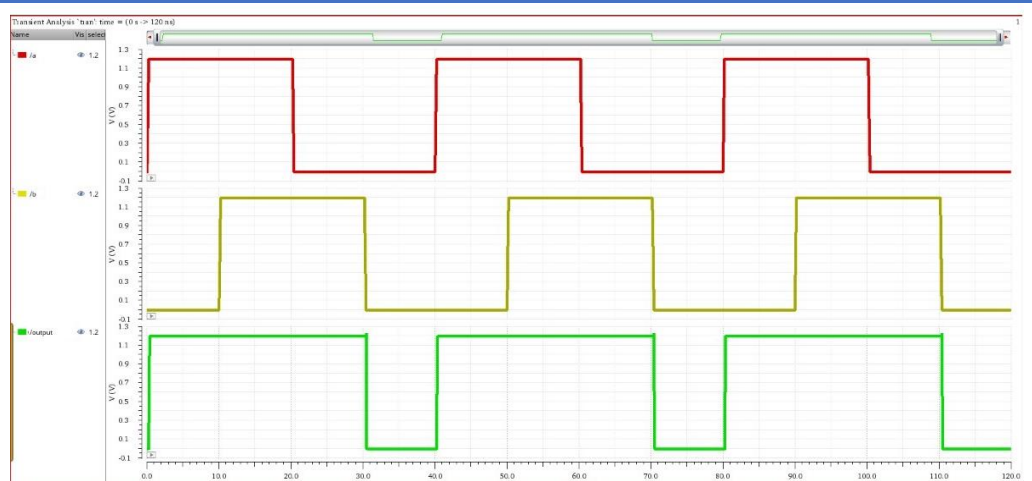

1100  
XOR



1101  
XNOR

 


1110  
NAND





1111  
NOR

 

## Delay and Power Consumption:

### Delay:

At worst-case (multiplication) between inputs of A = (1111) and B=(1111).

At Rising Edges:

$$t_{plh} = 425.3 \times 10^{-12} \text{ s}$$

$$t_{plh} = 425.3 \text{ ps}$$

| 1          |  |
|------------|--|
| Expression | (cross(value(VT("/y7") "Wp" 2e-06) 0.6 1 "rising" ...  |
| Value      | 425.3E-12  |
| Expression | (cross(value(VT("/y7") "Wp" 2e-06) 0.6 1 "falling" ... |
| Value      | 102.6E-12  |

At Rising Edges:

$$t_{phl} = 102.6 \times 10^{-12} \text{ s}$$


$$t_{phl} = 102.6 \text{ ps}$$

### Total propagation delay:

$$t_p = t_{phl} + t_{plh} = 2.639 \times 10^{-12}$$

$$t_p = 2.638 \text{ ps}$$

 Max Frequency should be =  $1 / 2t_p = 1.8942 \text{ GHz}$



### ***Power Consumption:***

*Total Current Drain from the supply Vdd =*

$$100.3 \times 10^{-6} \text{ A} = 100.3 \mu\text{A}$$

*Average power = total current x voltage of the output*

| <b><i>Outputs</i></b> | <b><i>Average power</i></b>             |
|-----------------------|---|
| <i>y0</i>             | <i>58.9 <math>\mu\text{watt}</math></i> |
| <i>y1</i>             | <i>12.4 <math>\mu\text{watt}</math></i> |
| <i>y2</i>             | <i>50.6 <math>\mu\text{watt}</math></i> |
| <i>y3</i>             | <i>58 <math>\mu\text{watt}</math></i>   |
| <i>y4</i>             | <i>62.8 <math>\mu\text{watt}</math></i> |
| <i>y5</i>             | <i>79.9 <math>\mu\text{watt}</math></i> |
| <i>y6</i>             | <i>53.6 <math>\mu\text{watt}</math></i> |
| <i>y7</i>             | <i>73.9 <math>\text{nwatt}</math></i>   |

## VHDL Code:

```
--Library decleration--
LIBRARY ieee;
USE ieee.STD_LOGIC_1164.ALL;
USE ieee.numeric_std.all;
USE ieee.std_logic_unsigned.all;

--ENTITY decleration of MUX--
ENTITY mux_16_1 is
PORT (
ip0MUX: in std_logic_vector (7 downto 0);
ip1MUX: in std_logic_vector (7 downto 0);
ip2MUX: in std_logic_vector (7 downto 0);
ip3MUX: in std_logic_vector (7 downto 0);
ip4MUX: in std_logic_vector (7 downto 0);
ip5MUX: in std_logic_vector (7 downto 0);
ip6MUX: in std_logic_vector (7 downto 0);
ip7MUX: in std_logic_vector (7 downto 0);
ip8MUX: in std_logic_vector (7 downto 0);
ip9MUX: in std_logic_vector (7 downto 0);
ip10MUX: in std_logic_vector (7 downto 0);
ip11MUX: in std_logic_vector (7 downto 0);
ip12MUX: in std_logic_vector (7 downto 0);
ip13MUX: in std_logic_vector (7 downto 0);
ip14MUX: in std_logic_vector (7 downto 0);
ip15MUX: in std_logic_vector (7 downto 0);
sel_16_1: in bit_vector (3 downto 0);
out_mux_16_1: out std_logic_vector (7 downto 0)
);
end mux_16_1;
--ENTITY decleration of MUX--
--ARCHITECTURE of MUX decleration--
ARCHITECTURE mux_op OF mux_16_1 is
BEGIN
ALUselection: process(sel_16_1, ip0MUX, ip1MUX , ip2MUX ,ip3MUX,ip4MUX,
ip5MUX,ip6MUX , ip7MUX,
ip8MUX, ip9MUX, ip10MUX , ip11MUX ,ip12MUX,ip13MUX, ip14MUX,ip15MUX)
BEGIN
--selection lines of the MUX--
case sel_16_1 is
when "0000" => out_mux_16_1 <= ip0MUX;
when "0001" => out_mux_16_1 <= ip1MUX;
when "0010" => out_mux_16_1 <= ip2MUX;
when "0011" => out_mux_16_1 <= ip3MUX;
when "0100" => out_mux_16_1 <= ip4MUX;
when "0101" => out_mux_16_1 <= ip5MUX;
when "0110" => out_mux_16_1 <= ip6MUX;
when "0111" => out_mux_16_1 <= ip7MUX;
when "1000" => out_mux_16_1 <= ip8MUX;
when "1001" => out_mux_16_1 <= ip9MUX;
when "1010" => out_mux_16_1 <= ip10MUX;
when "1011" => out_mux_16_1 <= ip11MUX;
when "1100" => out_mux_16_1 <= ip12MUX;
when "1101" => out_mux_16_1 <= ip13MUX;
when "1110" => out_mux_16_1 <= ip14MUX;
```

```

when "1111" => out_mux_16_1 <= ip15MUX;
end case;
end process ALUselection;
end mux_op;
--library decelrations--
LIBRARY ieee;
USE ieee.STD_LOGIC_1164.ALL;
USE ieee.numeric_std.all;
USE ieee.std_logic_unsigned.all;
--ENTITY ALU decleration--
ENTITY A_L_U is
PORT (
a :IN std_logic_vector(3 downto 0); --input a of 3 bits--
b :IN std_logic_vector(3 downto 0); --input b of 3 bits--
sel :IN bit_vector(3 downto 0); -- selection line-
y :OUT std_logic_vector(7 downto 0)
);
--ENTITY ALU decleration--
end A_L_U;
--Architecture decleration of A_L_U --
architecture operations of A_L_U is
--Signal deceleration--
signal
inc_a,dec_a,inc_b,dec_b,transfer_a,add_a_b,sub_a_b,compa,compb,and_op,or_op,x
or_op,xnor_op,nand_op,nor_op: std_logic_vector (7 downto 0);
signal multiply_ab: std_logic_vector (7 downto 0);
--Component decelration--
--16:1 Mux implementation--
component mux_16_1 is
port(
ip0MUX: in std_logic_vector (7 downto 0);
ip1MUX: in std_logic_vector (7 downto 0);
ip2MUX: in std_logic_vector (7 downto 0);
ip3MUX: in std_logic_vector (7 downto 0);
ip4MUX: in std_logic_vector (7 downto 0);
ip5MUX: in std_logic_vector (7 downto 0);
ip6MUX: in std_logic_vector (7 downto 0);
ip7MUX: in std_logic_vector (7 downto 0);
ip8MUX: in std_logic_vector (7 downto 0);
ip9MUX: in std_logic_vector (7 downto 0);
ip10MUX: in std_logic_vector (7 downto 0);
ip11MUX: in std_logic_vector (7 downto 0);
ip12MUX: in std_logic_vector (7 downto 0);
ip13MUX: in std_logic_vector (7 downto 0);
ip14MUX: in std_logic_vector (7 downto 0);
ip15MUX: in std_logic_vector (7 downto 0);
sel_16_1: in bit_vector (3 downto 0);
out_mux_16_1: out std_logic_vector (7 downto 0)
);
end component;
--Architecture BEGIN Operations --
begin
inc_a<= ("0000"& a(3 downto 0))+ "1"; --incerement a--
dec_a<= ("0000"& a(3 downto 0))- "1";--decrement a--
multiply_ab<=std_logic_vector(to_unsigned((to_integer(unsigned("0000"&
a))*to_integer(unsigned("0000"& b))),8));--multiplication--
inc_b<= ("0000"& b(3 downto 0))+ "1";--incerement b--

```

```

dec_b<= ("0000"& b(3 downto 0))-1;--decrement b--
transfer_a<=("0000"& a(3 downto 0));--transfer a--
add_a_b<=std_logic_vector(to_unsigned((to_integer(unsigned("0000"&
a))+to_integer(unsigned("0000"& b))),8));--add a and b--
sub_a_b<=std_logic_vector(to_unsigned((to_integer(unsigned("0000"& a))-
to_integer(unsigned("0000"& b))),8));--sub a and b--
compa <= ("0000"& not(a(3 downto 0)));--complimenet a--
compb <= ("0000"& not(b(3 downto 0)));--complimenet b--
and_op <= ("0000"&(a(3 downto 0) and b(3 downto 0)));--a and b--
or_op <= ("0000"&(a(3 downto 0) or b(3 downto 0)));--a or b--
xor_op <= ("0000"&(a(3 downto 0) xor b(3 downto 0)));--a xor b--
xnor_op <= ("0000"&(a(3 downto 0) xnor b(3 downto 0)));--a xnor b--
nand_op <= ("0000"&(a(3 downto 0) nand b(3 downto 0)));--a nand b--
nor_op <= ("0000"&(a(3 downto 0) nor b(3 downto 0)));--a nor b--
mux_1: mux_16_1 port map (ip0MUX => inc_a ,ip1MUX => dec_a,ip2MUX =>
multiply_ab,ip3MUX => inc_b,ip4MUX => dec_b,ip5MUX => transfer_a ,ip6MUX =>
add_a_b,ip7MUX => sub_a_b,
ip8MUX => compa, ip9MUX => compb, ip10MUX => and_op, ip11MUX => or_op,
ip12MUX => xor_op, ip13MUX => xnor_op, ip14MUX => nand_op, ip15MUX => nor_op,
sel_16_1=>sel, out_mux_16_1 => y);
end operations ;

```

## VHDL Test Benching:

```

--Testbench For A_L_U--
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
use ieee.std_logic_unsigned.all;
entity tb_ALU is
end tb_ALU;

architecture behaviour of tb_ALU is
component A_L_U
port( a :in std_logic_vector(3 downto 0);
b :in std_logic_vector(3 downto 0);
sel :in bit_vector(3 downto 0);
y :OUT std_logic_vector(7 downto 0)
);
end component;
signal a_test : std_logic_vector(3 downto 0) ;
signal b_test : std_logic_vector(3 downto 0) ;
signal sel_test : bit_vector(3 downto 0) ;
signal y_test : std_logic_vector(7 downto 0);    --output--
constant t : time := 50 ns;
begin
test: A_L_U port map (a => a_test, b => b_test, sel => sel_test, y =>
y_test);
TESTING: PROCESS
begin
a_test <= "1110";
b_test <= "0011";
sel_test <= "0000"; --Increment a--
wait for t;

```

```

sel_test <= "0001"; --Decrement a--
wait for t;
sel_test <= "0010";--Multiplication--
wait for t;
sel_test <= "0011";--Increment b--
wait for t;
sel_test <= "0100";--Decrement b--
wait for t;
sel_test <= "0101";--Transfer a--
wait for t;
sel_test <= "0110";--ADD--
wait for t;
sel_test <= "0111";--Subtract--
wait for t;
sel_test <= "1000";--Complement a--
wait for t;
sel_test <= "1001";--Complement b--
wait for t;
sel_test <= "1010";--And Gate--
wait for t;
sel_test <= "1011";--OR Gate--
wait for t;
sel_test <= "1100";--XOR Gate--
wait for t;
sel_test <= "1101";--XNOR Gate--
wait for t;
sel_test <= "1110";--Nand Gate--
wait for t;
sel_test <= "1111";--Nor Gate--
wait for t;
wait ; --wait forever--
end process ;
end behaviour;

```

| Wave - Default   |                  | Mags  |    |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|--|------------------|-------|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| <div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> </div> | /tb_alu/a_test   | 4'hE  | E  |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|  | /tb_alu/b_test   | 4'h3  | 3  |    |    |    |    |    |    |    |    |    |    |    |    |    |    |
|  | /tb_alu/sel_test | 4'h0  | 0  | 1  | 2  | 3  | 4  | 5  | 6  | 7  | 8  | 9  | A  | B  | C  | D  | E  |
|  | /tb_alu/y_test   | 8'h0F | 0F | 0D | 2A | 04 | 02 | 0E | 11 | 0B | 01 | 0C | 02 | 0F | 0D | 02 | 0D |